

CSE460

Lab Assignment 4


AHMAD AL ASAD

ID: 19101196


Section: 06

PROBLEM 1

Layout:


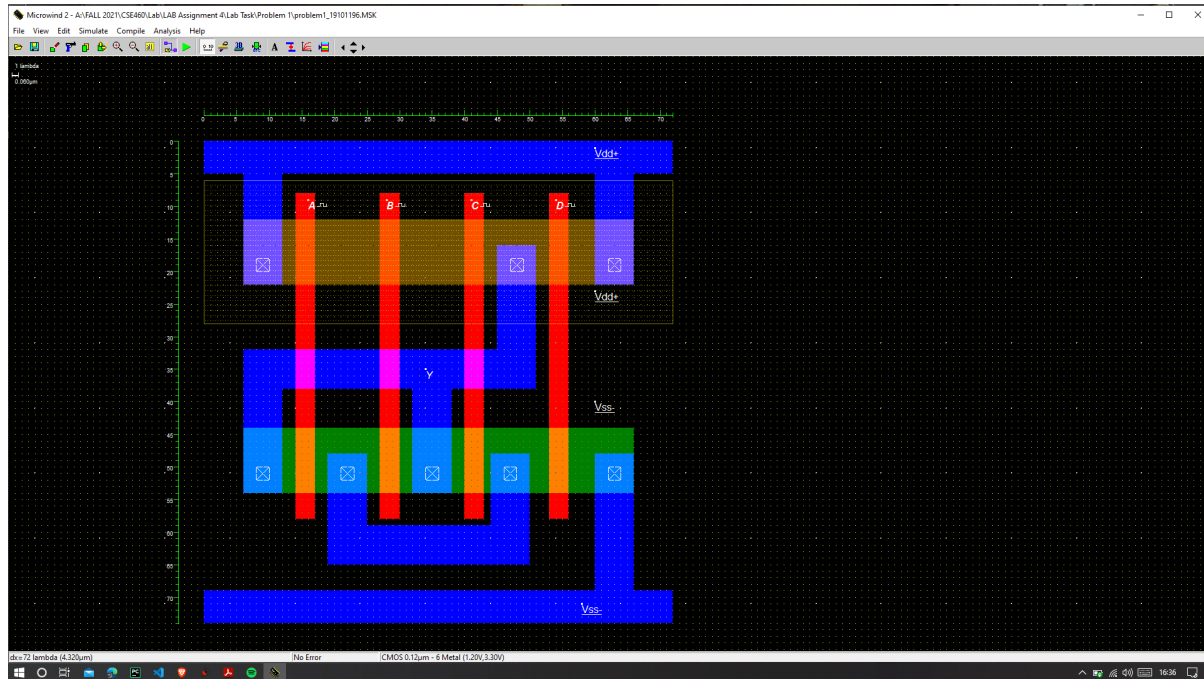


Timing Diagram:

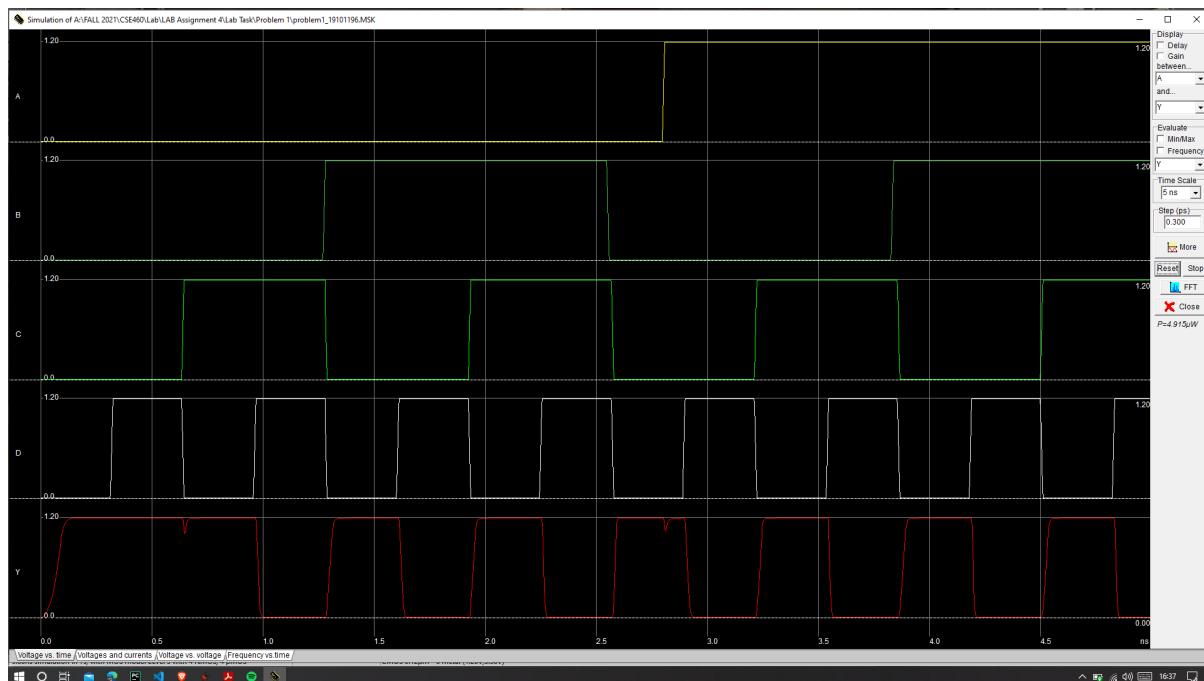

Problem 1:

$$Y = (A+B+C)D$$

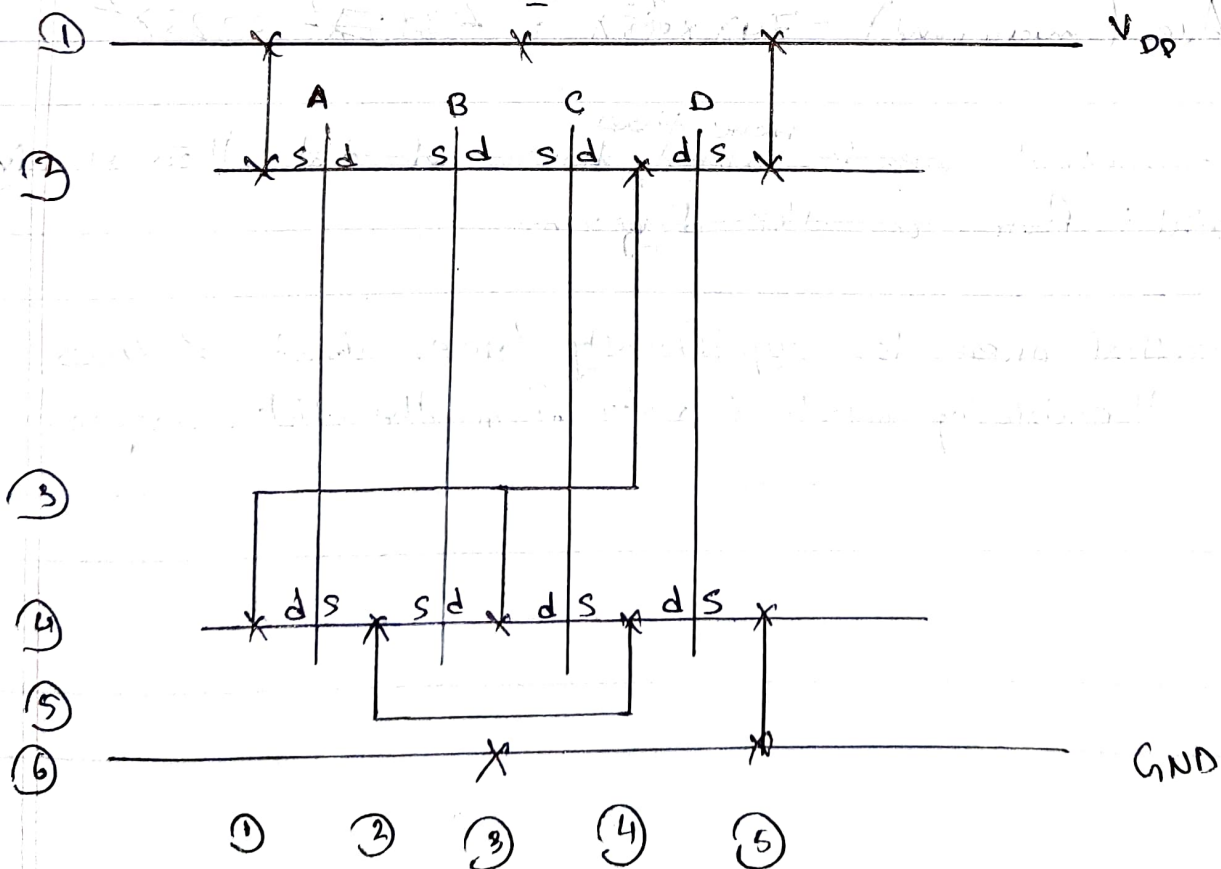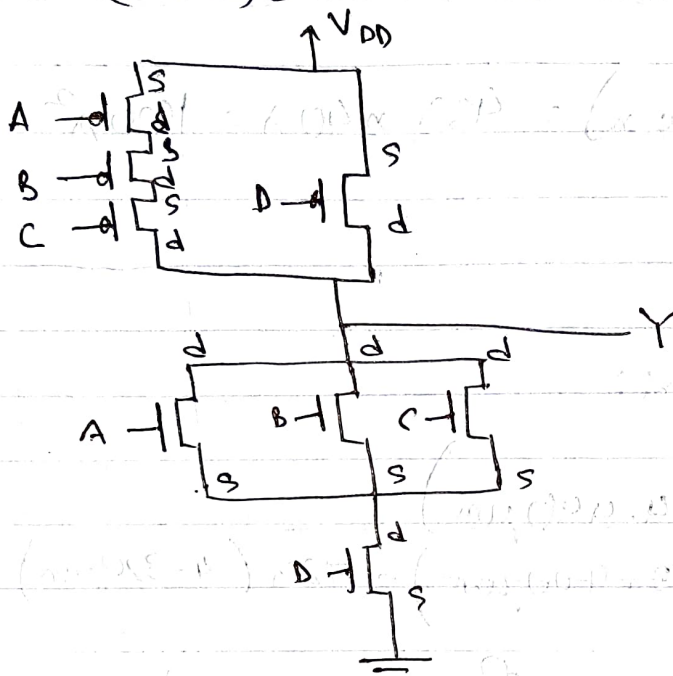

height: 6 tracks: $6 \times 8\lambda = 48\lambda$

width:

5 tracks: $5 \times 8\lambda = 40\lambda$

$$\text{Area (stick diagram)} = 48\lambda \times 40\lambda = 1920\lambda^2$$

From micrograph microwind:

$$dy = 74\lambda \left(4.440\mu\text{m} \right)$$

$$dx = \cancel{5\lambda (3.900\mu\text{m})} = 72\lambda (4.320\mu\text{m})$$

$$\text{Area (microwind)} = 74\lambda \times \cancel{5\lambda} = \cancel{4810\lambda^2} = 5328\lambda^2$$

The practical area is ^{more than} ~~almost~~ twice of that theoretically calculated from a stick diagram.

The practical area is significantly larger, almost 3 times of the theoretically calculated value from the stick diagram.

Truth Table


A	B	C	D	Y = $(A+B+C)D$
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

From timing diagram, between 0ns to 0.25ns , $A=0$, $B=0$, $C=0$, $D=0$. Then Y gives a high output 1. So, it matches the truth table.


Between 2.25ns to 2.5ns , $A=0$, $B=1$, $C=1$, $D=1$. Then Y gives low output 0. So, it matches the truth table.

PROBLEM 2

Layout:


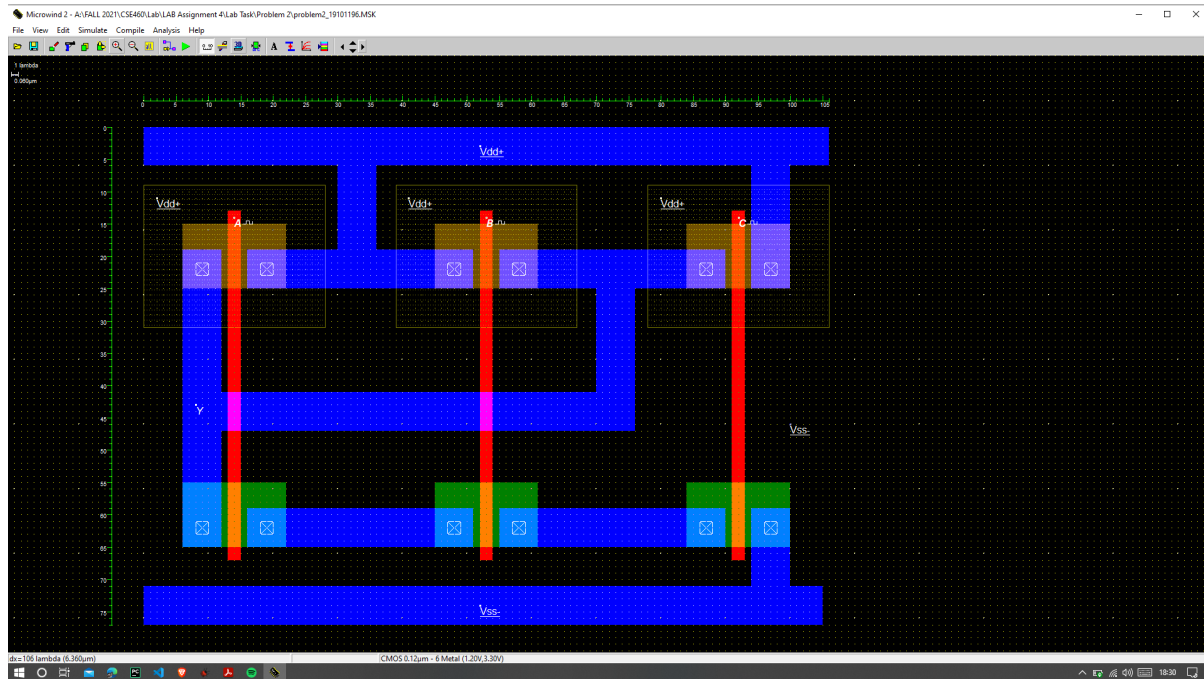


Timing Diagram:

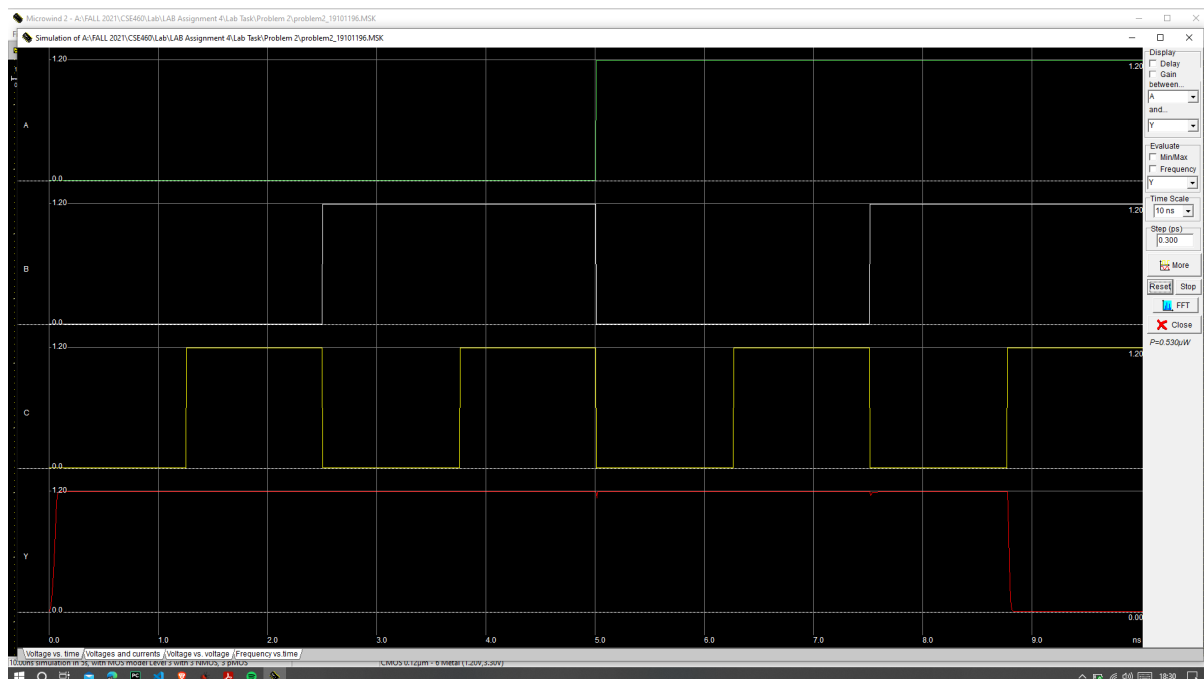

Problem 2:

$$Y = \overline{A \cdot B \cdot C}$$

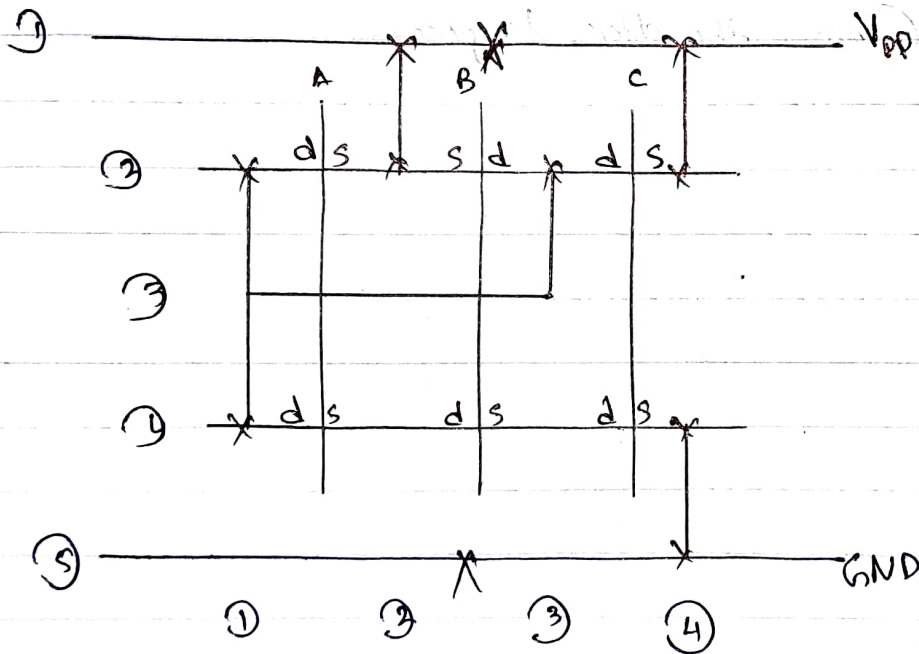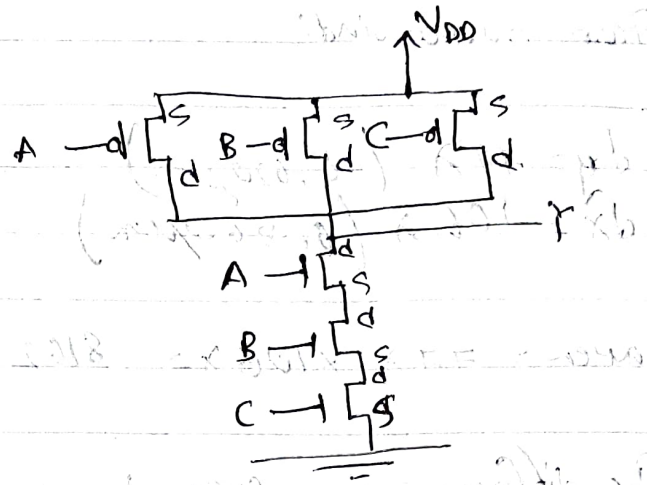

height: 5 tracks: $5 \times 8\lambda = 40\lambda$

width: 4 tracks: $4 \times 8\lambda = 32\lambda$

$\therefore \text{area} = 40\lambda \times 32\lambda = 1280\lambda^2$


From microwind?

$$dy = 77\lambda \quad (4.620\mu\text{m})$$

$$dx = 106\lambda \quad (6.360\mu\text{m})$$

$$\text{area} = 77\lambda \times 106\lambda = 8162\lambda^2$$

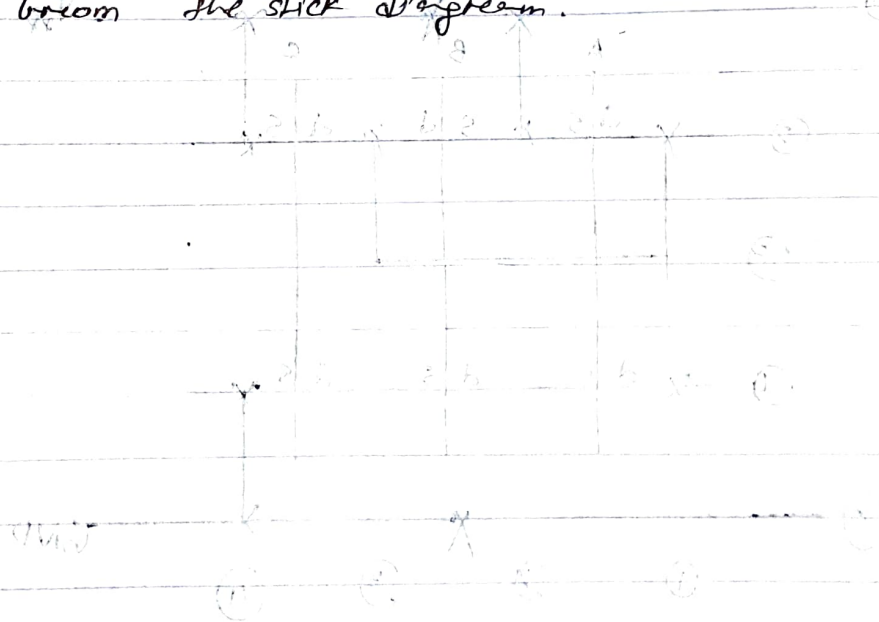The difference in area is a lot. The practical area from microwind is more than 6 times that of the theoretically calculated area from the stick diagram.



TOP: PRACTICAL AREA
 BOTTOM: THEORETICAL AREA
 (Note: The practical area is larger than the theoretical area)

Truth table

A	B	C	$Y = \overline{A \cdot B \cdot C}$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


From timing diagram:-

Between 1.25ns to 2.5ns, $A=0$, $B=0$, $C=1$. Then Y gives high output 1. So, it matches the truth table.


Between 8.75ns to 10ns, $A=1$, $B=1$, $C=1$. Then Y gives low output 0. So, it matches the truth table.

PROBLEM 3


Code:

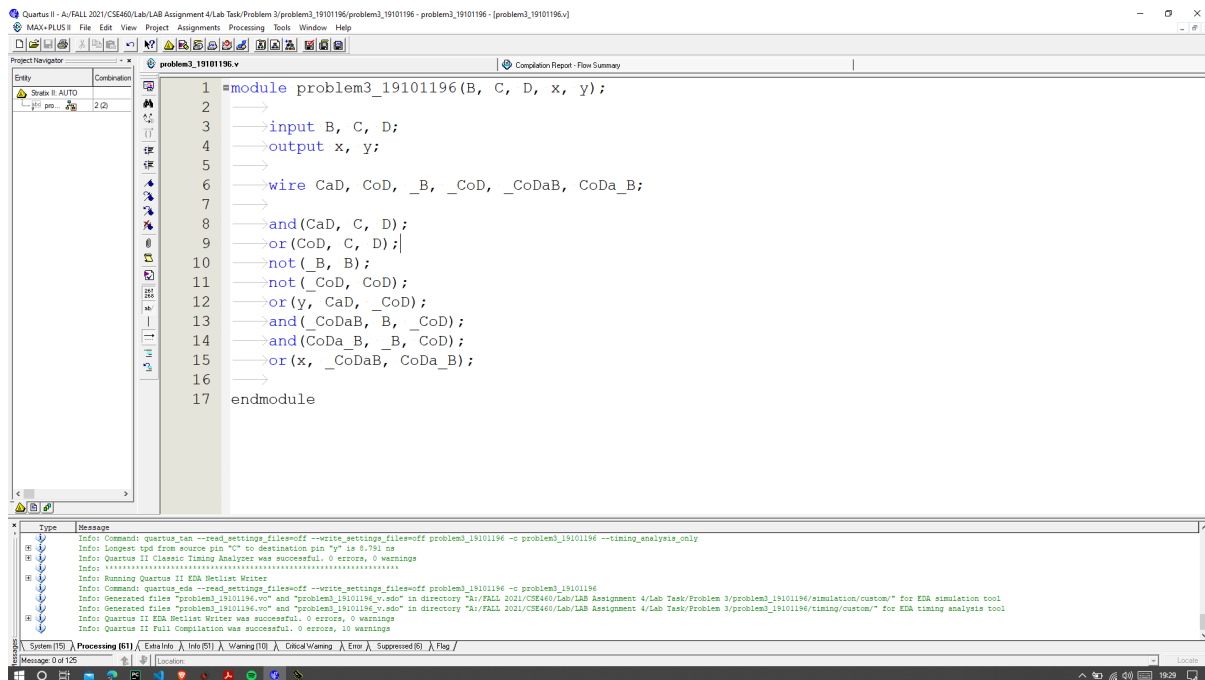


Compilation Report:

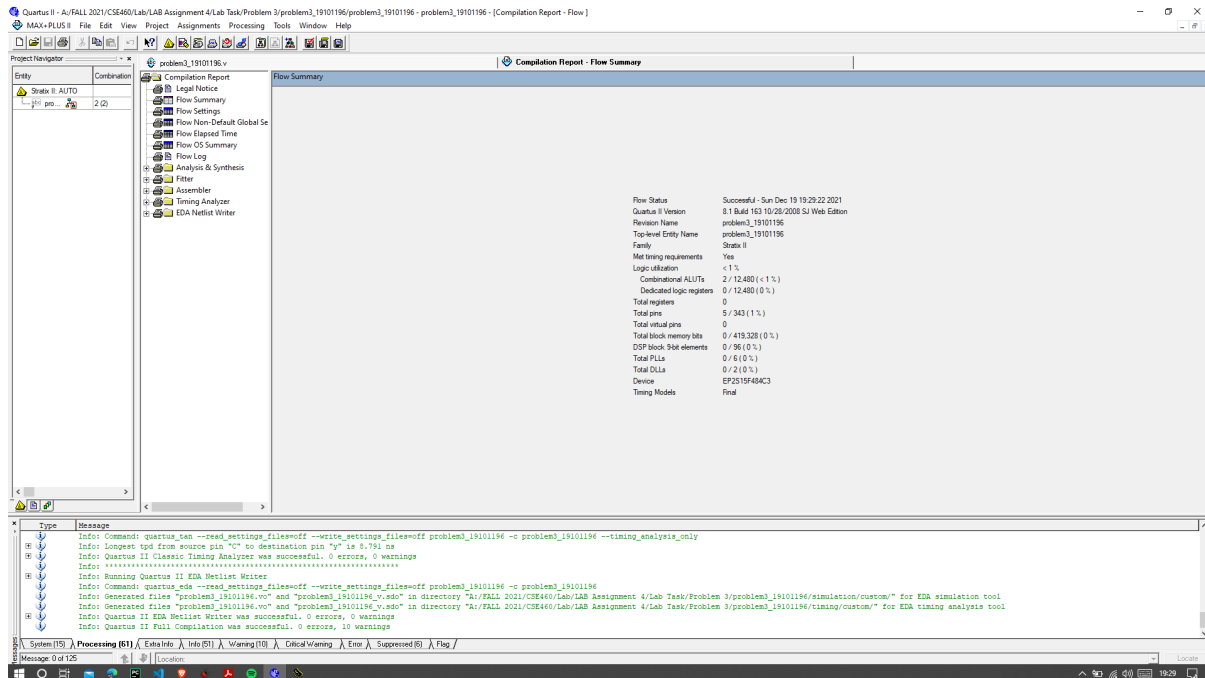


Layout:

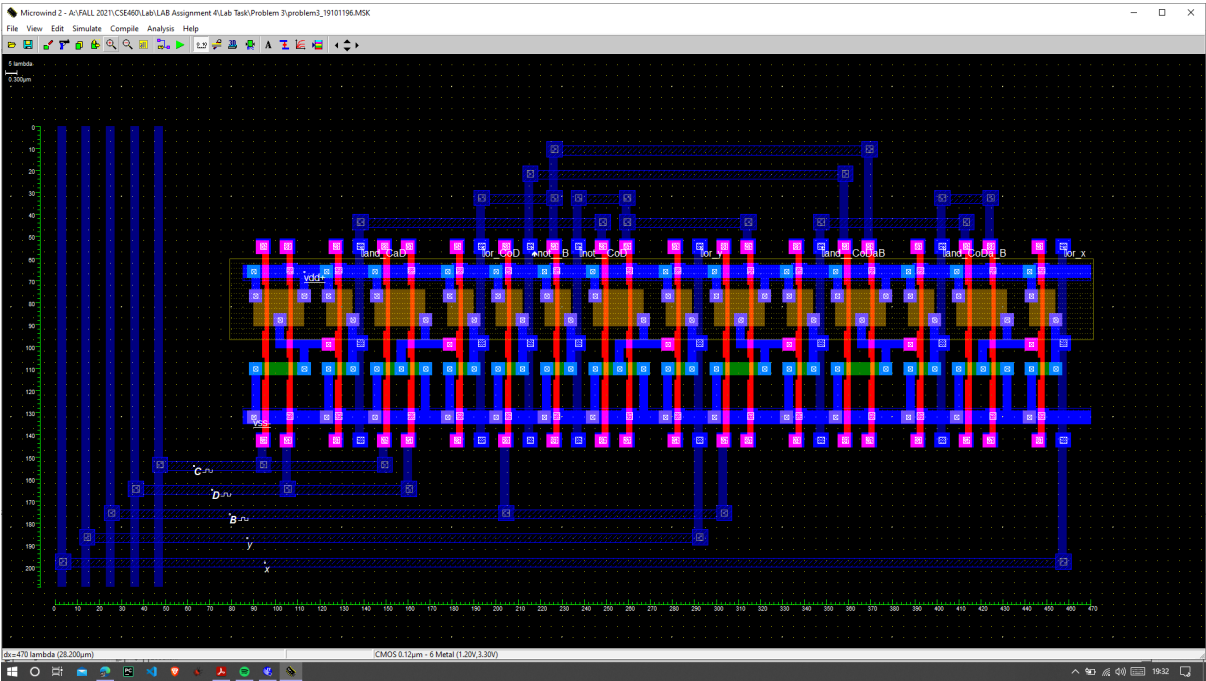

Timing Diagram:

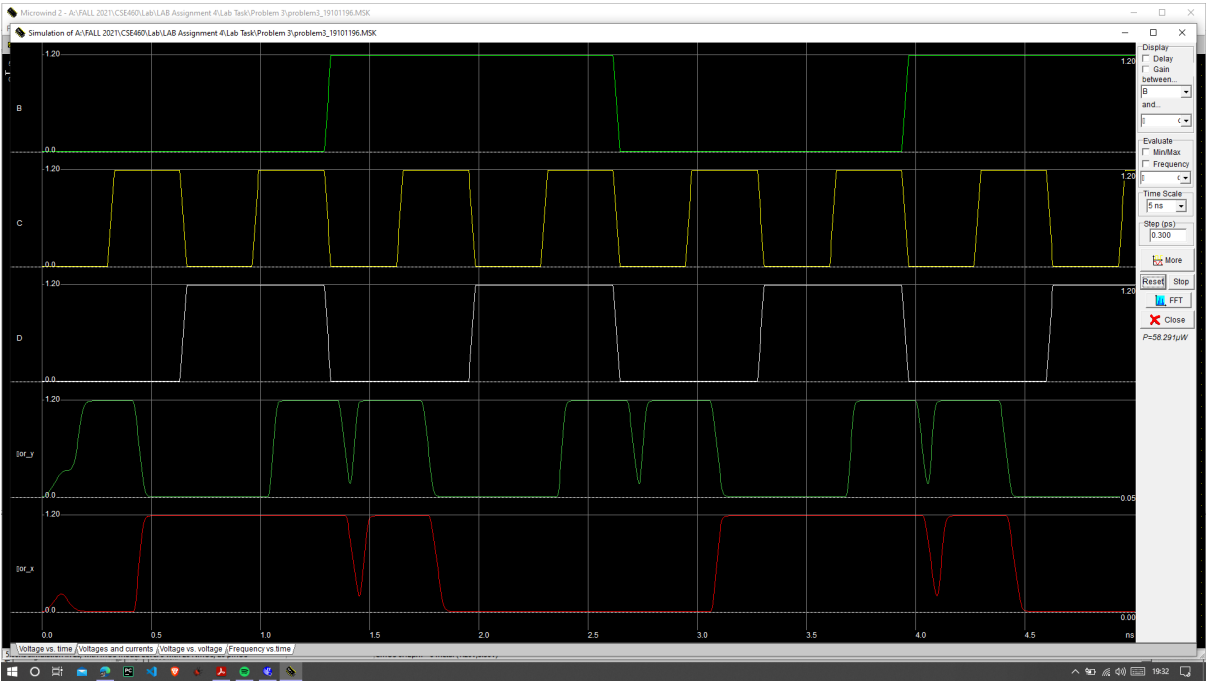

Problem 3

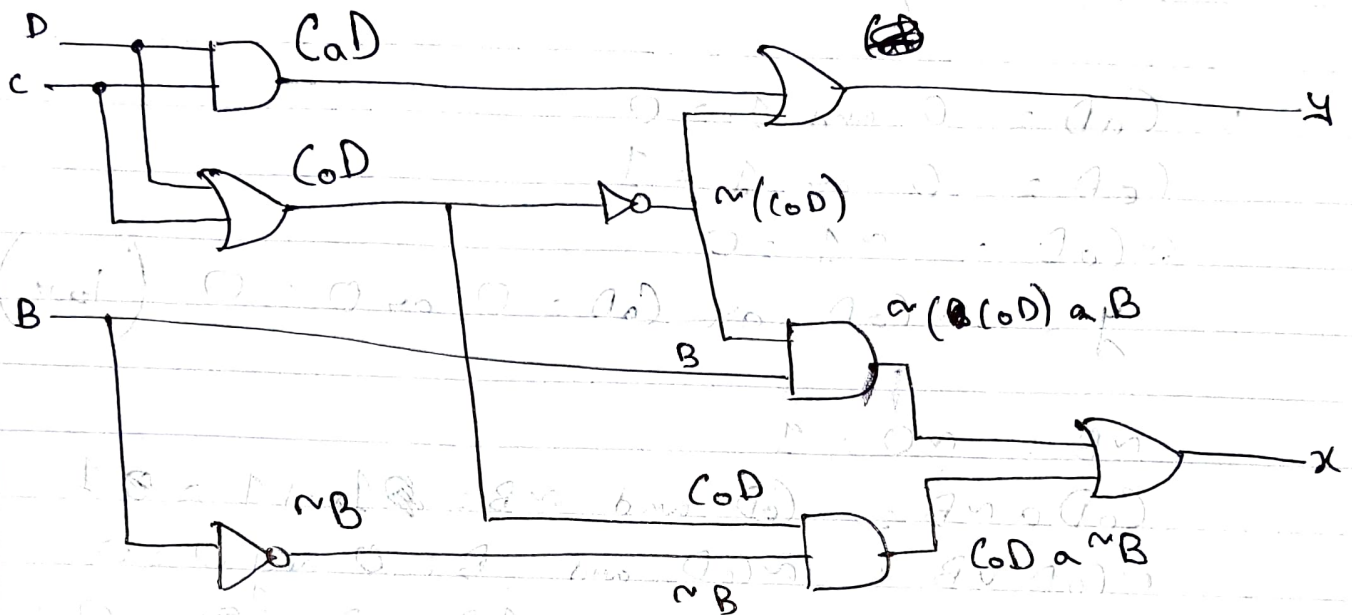

from microwind:

$$dy = 239\lambda \quad (14.340 \mu m)$$

$$dx = 469\lambda \quad (28.140 \mu m)$$

$$Area = 239\lambda \times 469\lambda = 112091\lambda^2$$

$$dy = 209\lambda \quad (12.540 \mu m)$$

$$dx = 470\lambda \quad (28.200 \mu m)$$

$$\begin{aligned} Area &= 209\lambda \times 470\lambda \\ &= 98230\lambda^2 \end{aligned}$$

From timing diagram, at time stamp 0.75 ns,

$$B = 0, C = 0, D = 1$$

$$\therefore C \wedge D = 0 \text{ and } 1 = 0$$

$$C \vee D = 0 \text{ or } 1 = 1$$

$$\sim(C \vee D) = \sim 1 = 0$$

$$y = \sim(C \vee D) \text{ or } C \wedge D = 0 \text{ or } 0 = 0 \text{ (low)}$$

$$\sim B = \sim 0 = 1$$

$$C \vee D \wedge \sim B = C \vee D \text{ and } \sim B = 1 \text{ and } 1 = 1$$

$$\sim(C \vee D) \wedge B = \sim(C \vee D) \text{ and } B = 0 \text{ and } 0 = 0$$

$$\therefore x = \sim(C \vee D) \wedge B \text{ or } C \vee D \wedge \sim B = 0 \text{ or } 1 = 1 \text{ (high)}$$

\therefore When $B = 0, C = 0, D = 1$,
output y gives low 0 and x gives high 1

\therefore The output from timing diagram matches the theoretical output.

At time stamp ~~4.25 ns~~, 3.75 ns,

$$B=0, C=1, D=1$$

$$C \wedge D = 1 \text{ and } 1 = 1$$

$$C \vee D = 1 \text{ or } 1 = 1$$

$$\sim C \vee D = \sim 1 = 0$$

$$y = \sim C \vee D \text{ or } C \wedge D = 1 \text{ or } 0 = 1 \text{ (High)}$$

$$\sim B = \sim 0 = 1$$

$$C \vee D \wedge \sim B = C \vee D \text{ and } \sim B = 1 \text{ and } 1 = 1$$

$$\sim C \vee D \wedge B = \sim C \vee D \text{ and } B = 0 \text{ and } 0 = 0$$

$$x = \sim C \vee D \wedge B \text{ or } C \vee D \wedge \sim B = 1 \text{ or } 0 = 1 \text{ (High)}$$

∴ When $B=0, C=1, D=1$,

output y gives high 1 and x gives high 1.

∴ The output from the timing diagram matches the theoretical output.